


# EE214 Digital Circuits Laboratory

## EXP6 – Sequence Generator

Swarup Dasharath Patil


22b3953

### RTL Viewer:

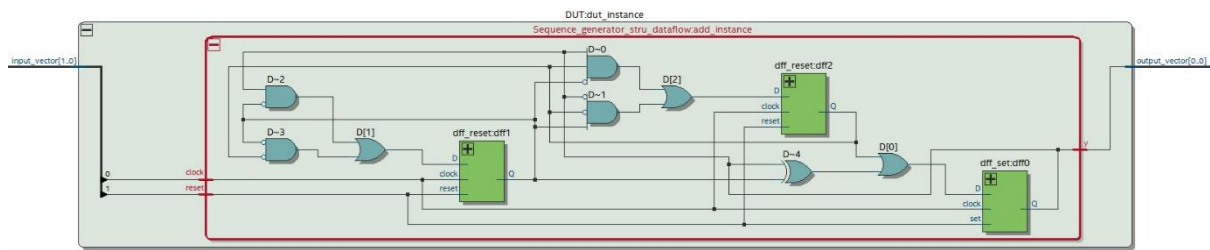


### RTL Simulation:

Note: SUCCESS, all tests passed.

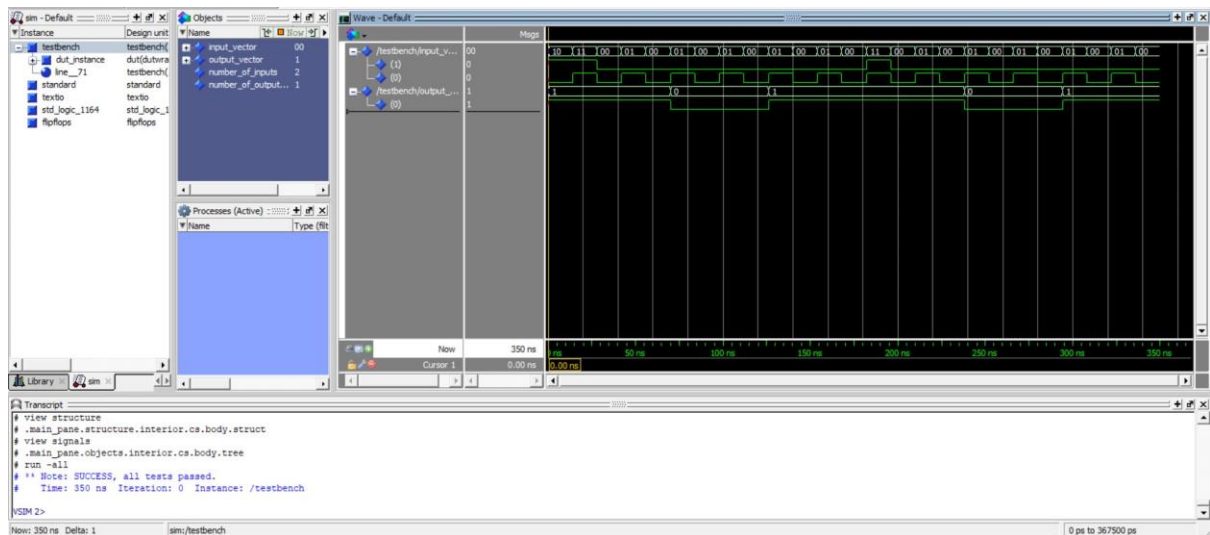

All tests were successful.

All tests were successful.

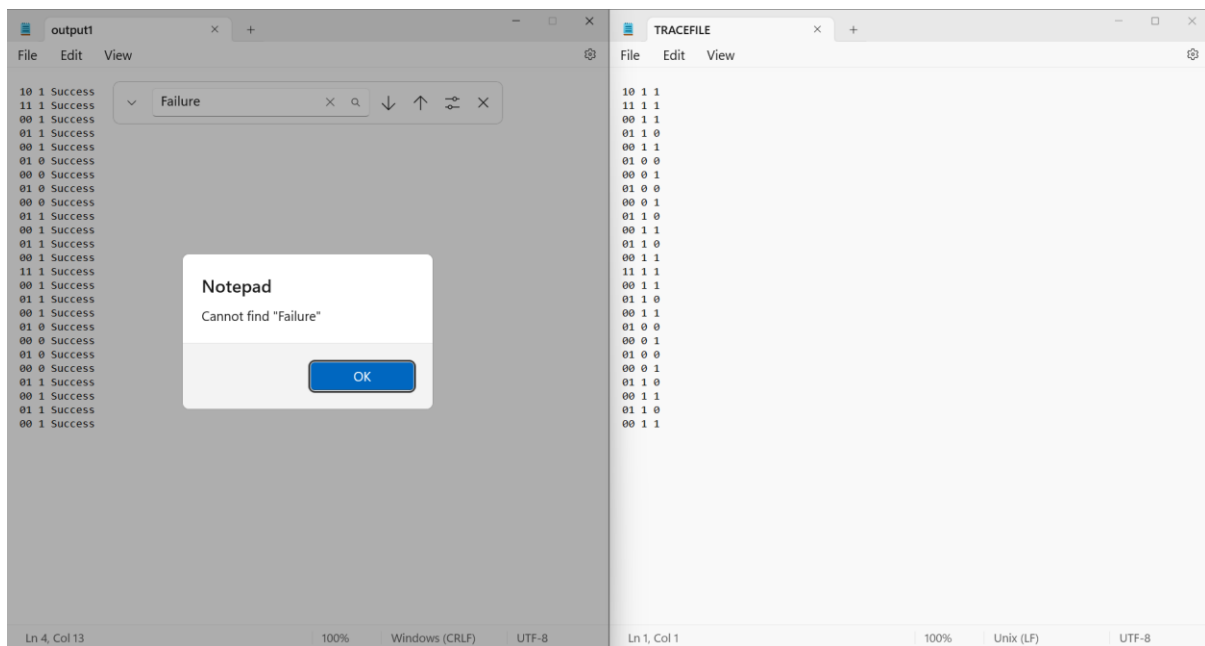

## Lab Journal:

A state diagram to generate the states so that LSB of the states will generate the required sequence and from the state table with the help of K-Maps generate equations for DFF inputs in terms of present state and reset verified by the TA.

Present State <small><math>Q_2, Q_1, Q_0</math></small>	Next State	DFF inputs <small><math>D_2, D_1, D_0</math></small>
001	011	0 1 1
011	000	0 0 0
000	010	0 1 0
010	101	1 0 1
101	111	1 1 1
111	011	0 1 1
100	011	0 1 1
110	011	0 1 1

$D_0$ :

$Q_2$	$Q_1$	$Q_0$	00	01	11	10
0	0	1	1	1	1	1
1	1	0	1	1	1	1

$$D_0 = Q_2 + \bar{Q}_0 Q_1 + Q_0 \bar{Q}_1$$

$$D_0 = Q_2 + (Q_0 \oplus Q_1)$$

$D_1$ :

$Q_2$	$Q_1$	$Q_0$	00	01	11	10
0	0	1	1	1	1	1
1	1	0	1	1	1	1


$$D_1 = Q_0 \bar{Q}_1 + \bar{Q}_1 \bar{Q}_2$$

$D_2$ :

$Q_2$	$Q_1$	$Q_0$	00	01	11	10
0	0	1	1	1	1	1
1	1	0	1	1	1	1

$$D_2 = \bar{Q}_1 Q_0 Q_2 + \bar{Q}_1 Q_1 \bar{Q}_2$$

Reset State

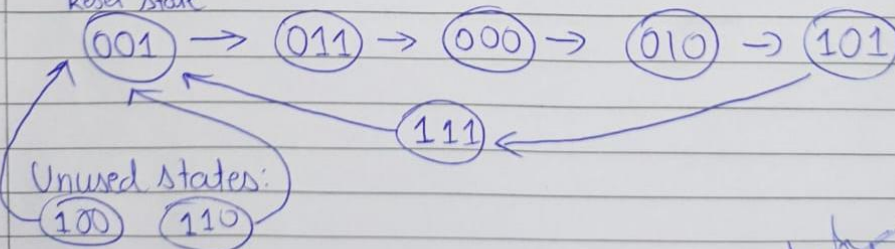

*Arjun*